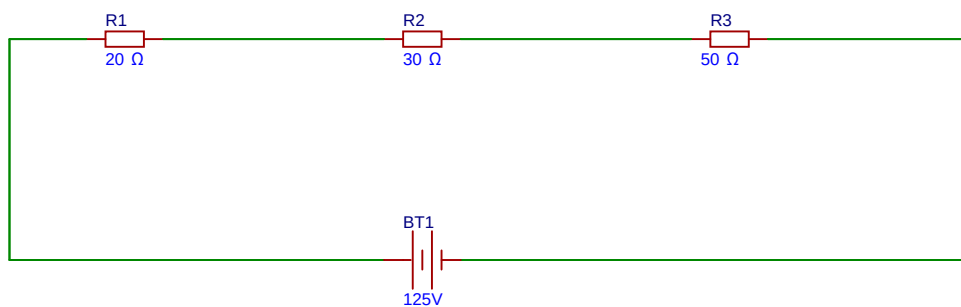




| Components            | Amount      |
|-----------------------|-------------|
| DC Power Supply (BT1) | 125V        |
| Resistor (R1)         | 20 $\Omega$ |
| Resistor (R2)         | 30 $\Omega$ |
| Resistor (R3)         | 50 $\Omega$ |

|                                                                                      |                  |                           |      |                |            |
|--------------------------------------------------------------------------------------|------------------|---------------------------|------|----------------|------------|
| Schematic                                                                            | Circuit A Series |                           |      | Create at      | 2026-05-09 |
|                                                                                      |                  |                           |      | Update at      | 2026-05-12 |
| Board                                                                                | Board1           |                           |      | Page           | P1         |
| Drawn                                                                                |                  | 166889 Circuit Design Lab |      |                |            |
| Reviewed                                                                             |                  |                           |      |                |            |
|                                                                                      |                  |                           |      |                |            |
|                                                                                      |                  | Version                   | Size | Page 1 Total 1 |            |
|  |                  | V1.0                      | A4   | EasyEDA.com    |            |